
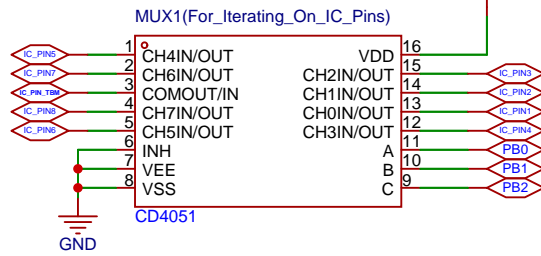



MUX 1 For Iterating On Pins

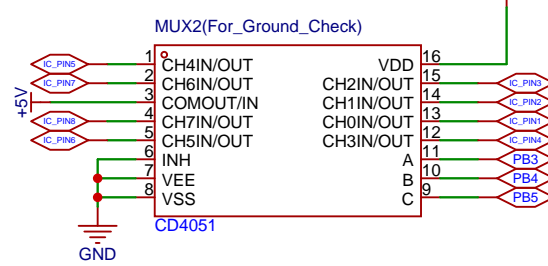



MUX 2 For Ground Check



IC To Be Tested

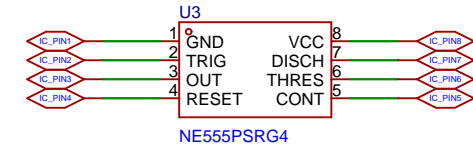

Diode Test Circuit

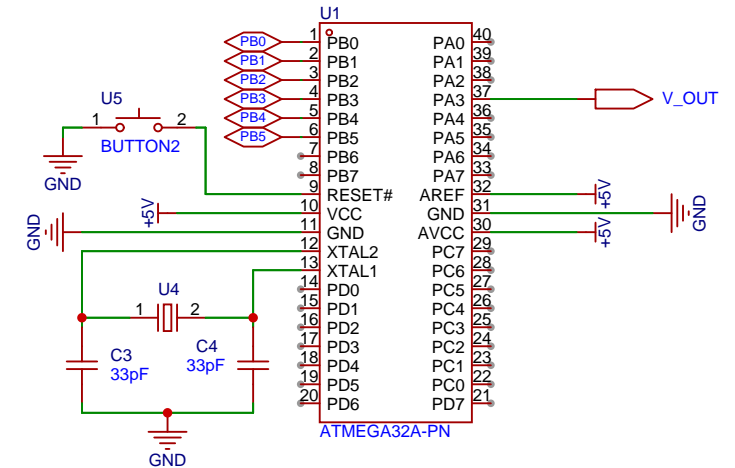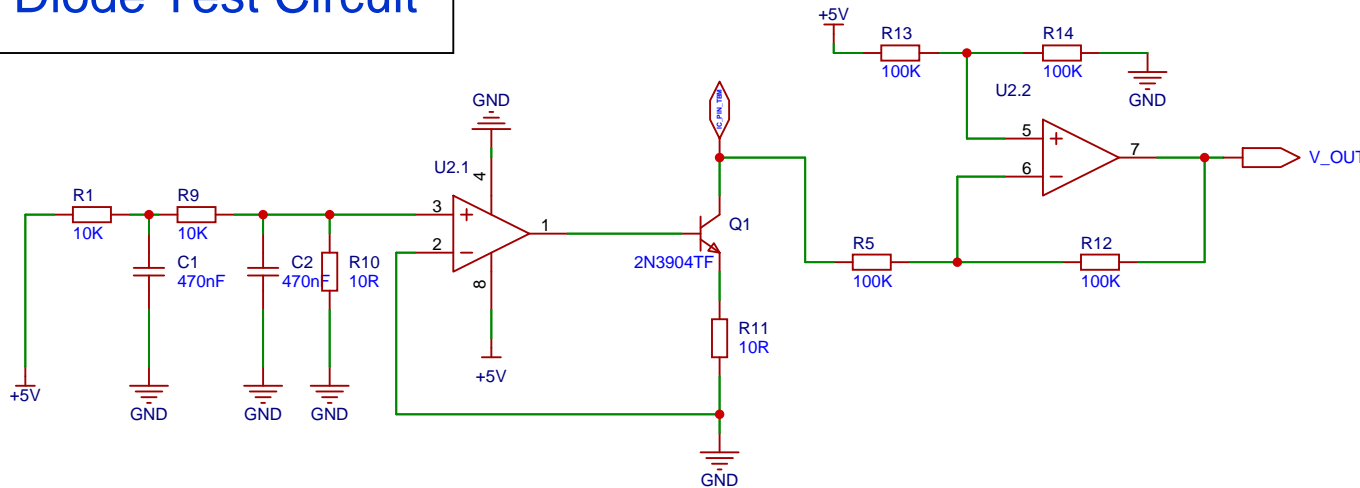

Instructor : Dr. Hossam El-Din Moustafa

Gasser Mohamed
Ahmed Mahfouz
Fares Farrag
Ahmed Hossam

Schematic	IC Tester			Create at	2026-01-02
Board	Board1			Update at	2026-01-03
Drawn	IC Tester			Page	P1
Reviewed					
			Version	Size	Page 1 Total 1
EasyEDA			V1.0	A4	EasyEDA.com